

Addis Ababa Institute of Technology

# Fundamental of Circuit

LAB REPORT 1

Biruk Misganaw

ATR/2035/08

## Table of Contents

<b>Introduction:</b>	2
<b>Pre-Lab preparation/Used Equipment:</b>	2
<b>Procedure:</b>	2
<b>Exercise 1:</b>	4
<b>Procedure:</b>	5
<b>Analysis/Result:</b>	5
<b>Calculation:</b>	5
<b>Conclusion:</b>	6
<b>Appendix I</b>	6

## Experiment No 1:

**Title:** Introduction to Electric Circuits Simulation and Testing


**Date** 19/4/2016

**Instructor Name:** Endrias Haile
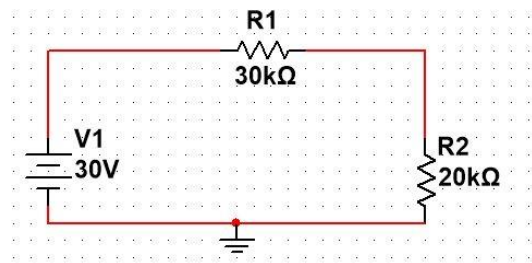
## Introduction:

The first lab was about Electric Circuits Simulation and Testing software called “Mutism”.

The general of goal of the first lab is to learn the basic user interface of the software. Such as, the toolbars, Circuit Window and etc. The first task was to draw simple circuit using the software and measured the corresponding current and voltage for the circuit.



Fig\_1

## Pre-Lab preparation/Used Equipment:

Before starting the lab, one must be sure that the computer which is ready for the experiment has already installed the Multisim software


## Procedure:

After making sure that the computer has a Multisim software. Let start drawing the simple circuit consists one voltage source, two resistor connected with series.

1. From components toolbar which contains Source button, Basic button, Diode button, Transistor button, select the source button and "Select a component" window will pop up




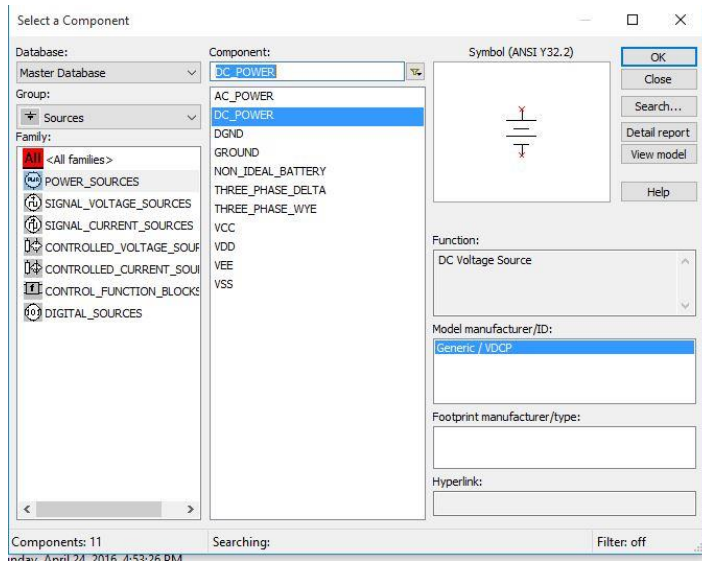2. On the "Select a component" window there is a search text field




Fig\_2

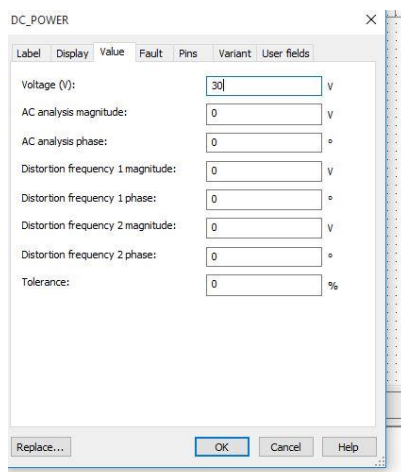3. Type "DC power" for source voltage, "Resistor" for resistor, "DC current" for current
4. First search for "DC power" double click in it and the window show below shown up and se the value to 30




Fig\_3

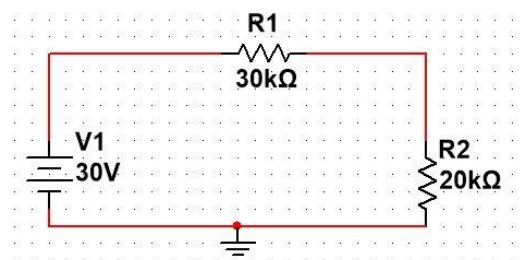5. Using the same procedure for resistor and ground and connecting them with the red wire you can draw the circuit shown below



Fig\_4

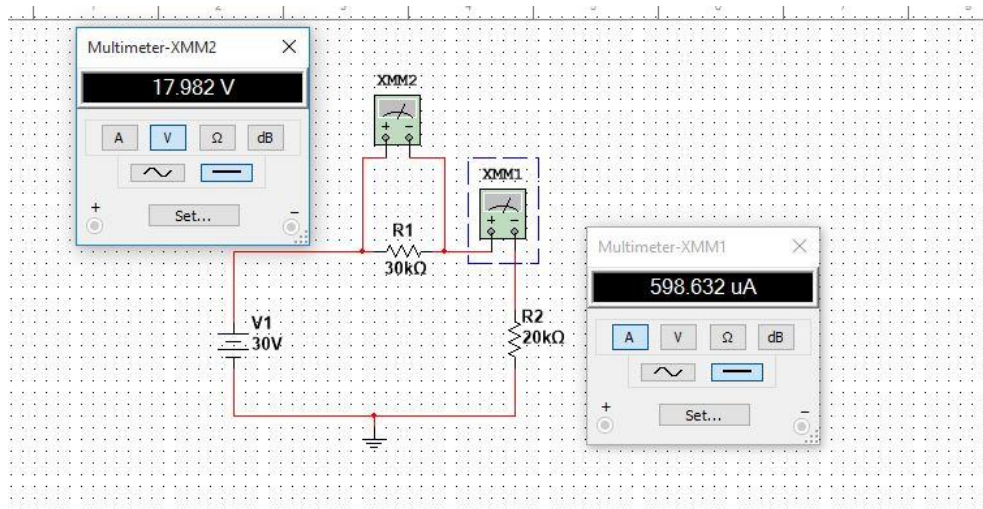
6. Then to measure the current and voltage across the circuit from instrument toolbar select "Multimeter" and connect it between R1 and R2 to measure the current. Connect the Multimeter with parallel to R1 to measure the voltage.



Fig\_5

### Exercise 1:

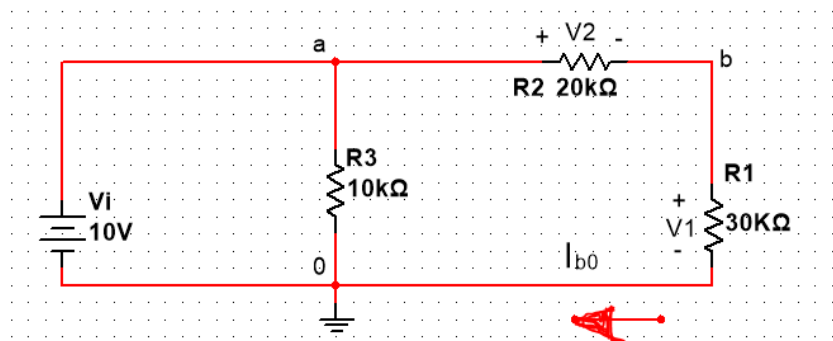
1. Build the circuit of Fig. 1 in NI Multisim 13.0.
2. Connect a voltmeter between nodes „a“ and „b“.
3. Connect an ammeter for the measurement of  $I_{b0}$ .



Fig\_6


### Procedure:

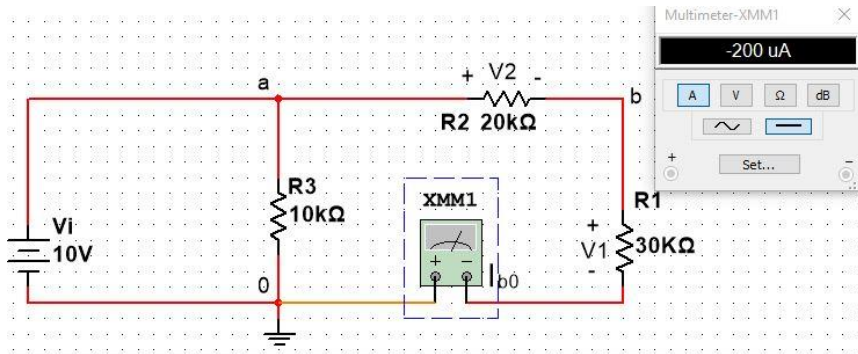1. Following the step on the procedure 1 you can draw the circuit given above
2. Measurement
  - a. To measure the current in  $I_{b0}$  put a Multimeter between the ground and R1.



Fig\_7

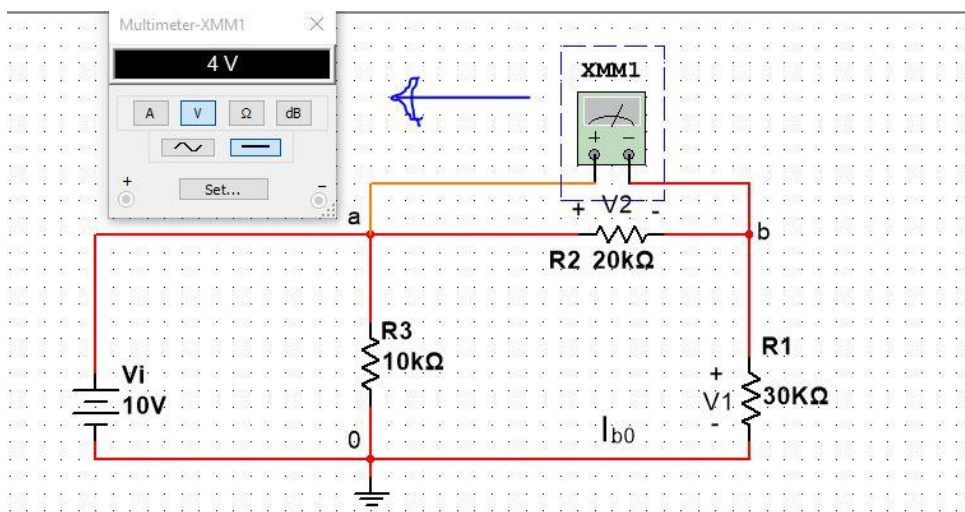- b. To measure the voltage at R2 connect a Multimeter at node 'a' and node 'b'



Fig\_8

### Analysis/Result:

In this section it's been looked that the comparison between the calculated values for the circuit and the actual measurements we got by using the Multimeter in series and in parallel with the different parts of the circuit have been summarized by Hand calculation and the table below

### Calculation:

#### 1. Calculate $I_{b0}$ x

From 0 – a – 0 loop

$$-10v + R3(i3) = 0$$

$$-10 + 10(i3) = 0$$

$$I_3 = 1 \text{ mA}$$

From a-b-0 loop

$$-10k(1mA) + 20k(I_{b0}) + 30k(I_{b0}) = 0$$

$$I_{b0} = 0.2A$$

## 2. Calculate $V_2$

$$V_2 = R_2 \cdot I_{b0}$$

$$V_2 = 20K \cdot 0.2A$$

$$V_2 = 4V$$

	$I_{b0}$	$V_2$
Measured	-0.2A	4V
Calculated	0.2A	4V

Table\_1

## Conclusion:

As it can be inferred from the above tables, (table 1) most of the measured values are more or less close to their respective calculated values. However, the current is negative on the measured value but it can be taken as positive because it's only a matter of polarity. The current is positive when the direction changed.

## Appendix I

$$V_2 = 4$$

$$I_{b0} = -0.2A$$